
 


VERILOG ASSIGNMENT

3 BIT BINARY MULTIPLIER

```
module bitmultiplier3(input [2:0]A,B,
output reg [5:0]P);
always@(*)
P=(A*B);
Endmodule

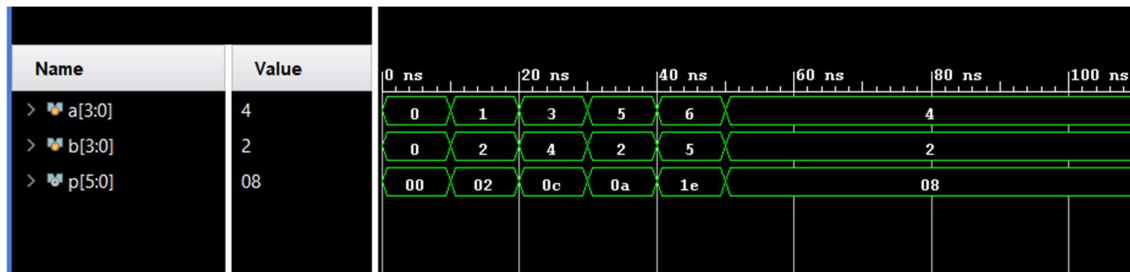module multiplierbit3_tb();
reg [3:0]a,b;
wire [5:0]p;
bitmultiplier3 dut (a,b,p);
initial
begin
a=3'b000;b=3'b000;#10;
a=3'b001;b=3'b010;#10;
a=3'b011;b=3'b100;#10;
a=3'b101;b=3'b010;#10;
a=3'b110;b=3'b101;#10;
a=3'b100;b=3'b010;#10;
$display("a=%0b,b=%0b,p=%0b",a,b,p);
#50;
$stop;
end
endmodule
```



2.BINARY ADDER

```

module bcd_adder(
input [3:0] A, input [3:0] B, input Cin,
    output reg [3:0] Sum, output reg Cout);
reg [4:0] temp_sum;
  
```

```
always @(*) begin
    temp_sum = A + B + Cin;
    if (temp_sum > 9) begin
        temp_sum = temp_sum + 6;
        Cout = 1;
    end else Cout = 0;
    Sum = temp_sum[3:0];
end
endmodule
```

```
module bcd_adder_tb();
    reg [3:0] A, B;
    reg Cin;
    wire [3:0] Sum;
    wire Cout;
```

```
    bcd_adder dut (.A(A), .B(B), .Cin(Cin), .Sum(Sum), .Cout(Cout));
```

```
    initial begin
        $display("Time\tA\tB\tCin\t|\tSum\tCout");
        $monitor("%0t\t%0d\t%0d\t%0b\t|\t%0d\t%0b", $time, A, B, Cin,
            Sum, Cout);
        A=4'd2; B=4'd3; Cin=0; #10;
        A=4'd5; B=4'd4; Cin=0; #10;
```

```

A=4'd6; B=4'd7; Cin=0; #10;

A=4'd8; B=4'd5; Cin=1; #10;



A=4'd9; B=4'd9; Cin=0; #10;

$display("Simulation Completed."); $finish;

end

endmodule

```

 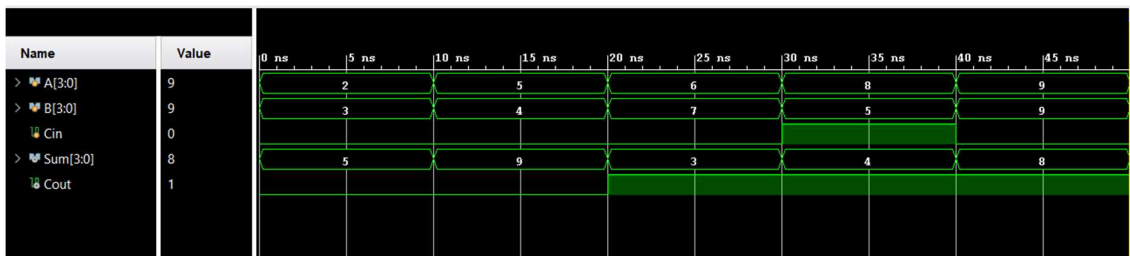

INVERTER USING BASIC GATES

```

module inverter_basicgates(input a,
output reg and_out,output reg or_out,output reg not_out,output reg
nand_out,output reg xor_out,output reg xnor_out);

reg a_bar;



always@(*)

begin
a_bar=~a;

```

```
and_out=a_bar&1'b1;
or_out=a_bar|1'b0;
not_out=~a;
nand_out=~(a_bar&1'b1);
xor_out=a^1'b1;
xnor_out=~(a^1'b1);
end
endmodule
```
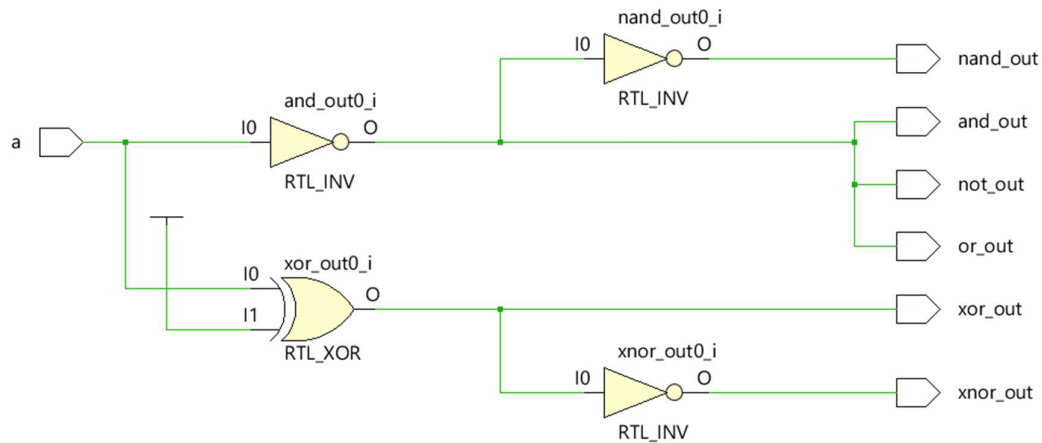 
```
module invereter_tb();
reg A;
wire
AND_OUT,OR_OUT,NOT_OUT,NAND_OUT,XOR_OUT,XNOR_OUT;
inverter_basicgates
dut(A,AND_OUT,OR_OUT,NOT_OUT,NAND_OUT,XOR_OUT,XNOR_O
UT);
initial
begin
A=1'b1;#10;
A=1'b0;
end
endmodule
```



BUFFER USING BASIC GATES

```

module buffer_gates(input a,output reg
and_out,or_out,not_out,xor_out,xnor_out);
always@(*)
begin
and_out=a&1'b1;
or_out=a|1'b0;
not_out=~(a);
xor_out=a^1'b0;
xnor_out=~(a^1'b0);
end

```

```
endmodule
```

```
module buffer_tb();
```

```
reg A;
```

```
wire AND_OUT,OR_OUT,NOT_OUT,XOR_OUT,XNOR_OUT;
```

```
buffer_gates dut (A,AND_OUT,OR_OUT,NOT_OUT,XOR_OUT,XNOR_OUT);
```

```
initial
```

```
begin
```

```
A=1'b1;#10;
```



```
A=1'b0;
```

```
#10;
```

```
$finish;
```

```
end
```

```
endmodule
```

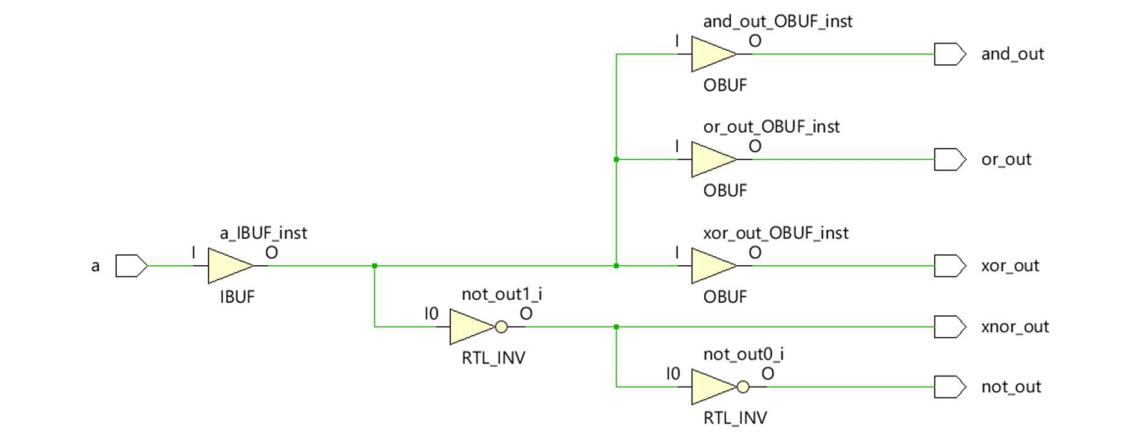
 


BCD TO 7 SEGMENT DISPLAY

```
module bcd_7_segment(input[3:0] bcd,output reg [6:0]seg);
always@(*)
begin
case(bcd)
4'b0000:seg=7'b1111110;
4'b0001:seg=7'b0110000;
4'b0010:seg=7'b1101101;
4'b0011:seg=7'b1111001;
4'b0100:seg=7'b0110011;
4'b0101:seg=7'b1011011;
4'b0110:seg=7'b1011111;
4'b0111:seg=7'b1110000;
4'b1000:seg=7'b1111111;
4'b1001:seg=7'b1111011;
default:seg=7'b0000000;
endcase
end
endmodule
```

```
module bcd_7_seg_tb();
reg [3:0]BCD;
wire[6:0]SEG;
```
  
```
bcd_7_segment dut (BCD,SEG);  
initial  
begin  
BCD=4'd0;#10;  
BCD=4'd1;#10;  
BCD=4'd2;#10;  
BCD=4'd3;#10;  
BCD=4'd4;#10;  
BCD=4'd5;#10;  
BCD=4'd6;#10;  
BCD=4'd7;#10;  
BCD=4'd8;#10;  
BCD=4'd9;#10;  
BCD=4'd10;#10;  
BCD=4'd11;#10;  
BCD=4'd12;#10;  
BCD=4'd13;#10;  
BCD=4'd14;#10;  
BCD=4'd15;#10;  
$monitor("BCD=%0b,SEG=%0b",BCD,SEG);  
$finish;  
end  
endmodule
```



24 HOUR TIMER

```

module timer_24(input clk,rst,
output reg [4:0]hours,
output reg [5:0]minutes,
output reg [5:0]seconds);
always@(posedge clk or posedge rst)
if (rst)
begin
hours<=0;
minutes<=0;
seconds<=0;
end
else
begin
if(seconds==59)
begin

```

```
seconds<=0;
if(minutes==59)
begin
minutes<=0;
if(hours==23)
hours<=0;
else
hours<=hours+1;
end else
begin
minutes<=minutes+1;
end
end
else
begin
seconds<=seconds+1;
end
end
endmodule
```

```
module timer_24_tb( );
reg CLK,RST;
wire[4:0]HOURS;
wire[5:0]MINUTES,SECONDS;
timer_24 dut(CLK,RST,HOURS,MINUTES,SECONDS);
initial
```

```

begin
CLK=0;

forever #5 CLK=~CLK;

end

initial
begin
$display("CLK=%0b,RST=%0b,HOURS=%0b,MINUTES=%0b,SECONDS=%0b",CLK,
RST,HOURS,MINUTES,SECONDS);

RST=1;#10;RST=0;

repeat(3700)@(posedge CLK);

RST=1;#10;RST=0;

repeat(10)@(posedge CLK);


$display("simulation complete");


$finish;

end

endmodule

```

 

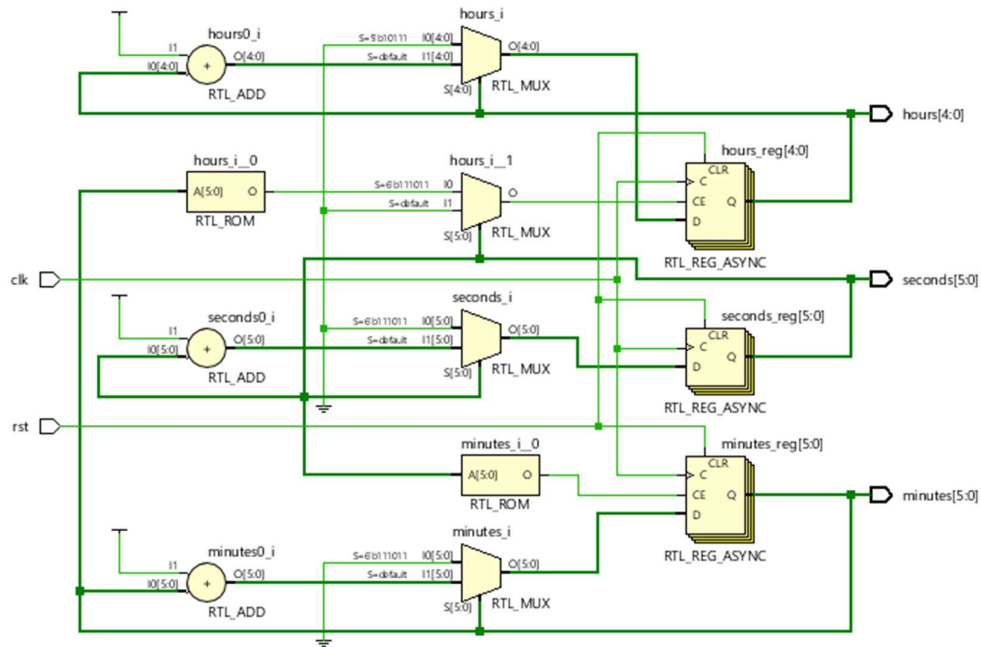

2 FLIPFLOP SYNCHRONIZER

```

module two_ff_synch(input wire clk, input wire async_in,
    output reg sync_out);
    reg sync_ff1;
    always @(posedge clk) begin
        sync_ff1 <= async_in;
        sync_out <= sync_ff1;
    end
endmodule

```

```

module two_ff_syn_tb();
    reg clk, async_in;
    wire sync_out;

    two_ff_synch dut (clk, async_in, sync_out);

```

```
initial begin
```

```
    clk = 0; forever #5 clk = ~clk;
```

```
end
```

```
initial begin
```

```
    $display("Time\tclk\tasync_in\tsync_out");
```

```
    $monitor("%0t\t%b\t%b\t\t%b", $time, clk, async_in, sync_out);
```

```
    async_in = 0; #20;
```

```
    #7 async_in = 1;
```

```
    #13 async_in = 0;
```

```
    #9 async_in = 1;
```

```
    #6 async_in = 0;
```

```
    #15 async_in = 1;
```

```
    #11 async_in = 0;
```

```
    #20 async_in = 1;
```

```
    #30 async_in = 0;
```



```
    #40;
```

```
    $display("Simulation Complete.");
```

```
    $finish;
```

```
end
```

```
endmodule
```

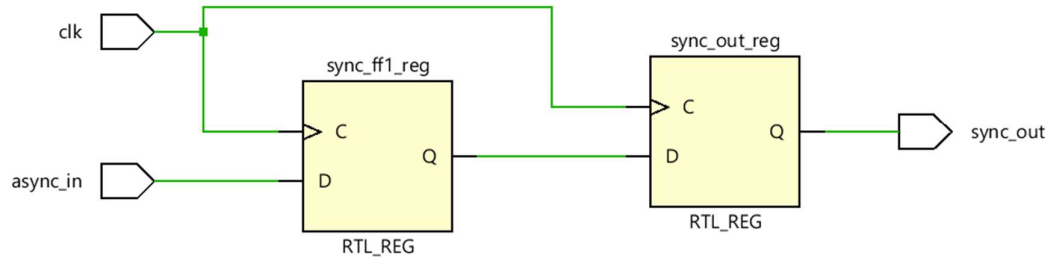 

MOD 5 UPCOUNTER WITH 50% DUTY CYCLE

```

module mod5 (input clk, rst,
output reg q);
reg [2:0] count;
always @(posedge clk or negedge rst)
begin
if (!rst) begin
count <= 3'd0;
q <= 1'b0;
end else begin
if (count == 3'd4)
count <= 3'd0;
else



```



```
count <= count + 3'd1;
if (count == 3'd0 || count == 3'd2)
    q <= ~q;
end
end
endmodule
```

```
module mod_5_tb();
reg CLK,RST;
wire Q;
mod5 dut (CLK,RST,Q);
initial
begin
    CLK=0;
    forever #5 CLK=~CLK;
end
initial
begin
    RST=1'b0;
    #10;
    RST=1'b1;
    #100;
    $display("CLK=%0b,RST=%0b,Q=%0b",CLK,RST,Q);
    #10;
    $stop();
end
```

endmodule

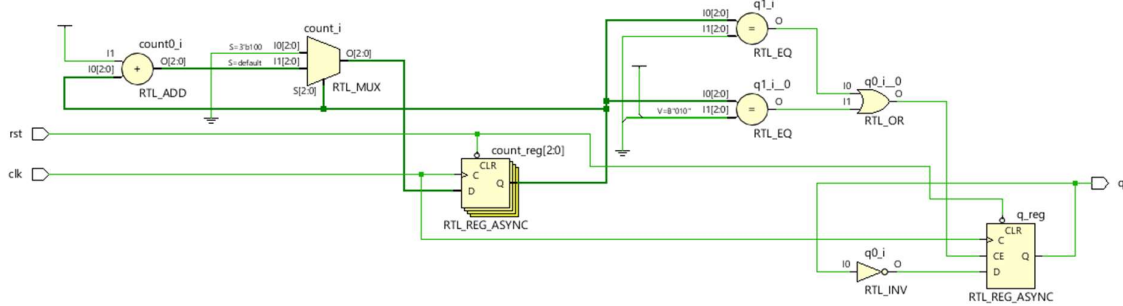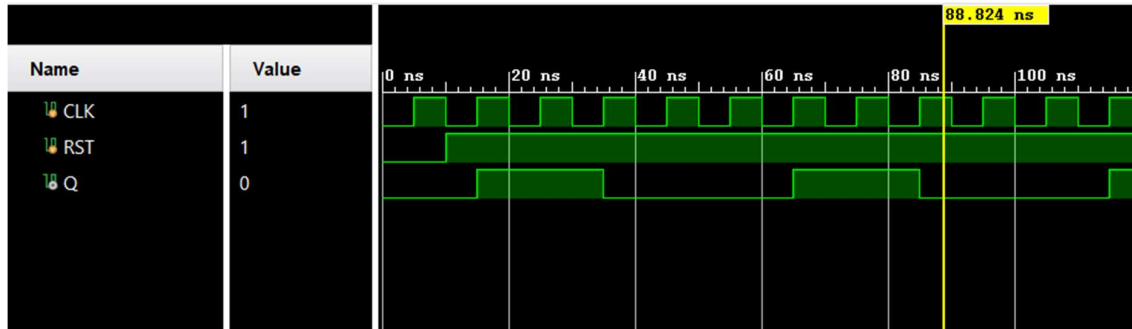

AUTOMATIC DOOR OPENING

```
Module automatic_door(clk,rst,sensor,timer,motor_out);
```

```
input clk,rst,sensor,timer;
```

```
output reg motor_out;
```

```
reg [1:0]ps,ns;
```

```
parameter closed=2'b00,opening=2'b01,open=2'b10,closing=2'b11;
```

```
always@(posedge clk) //reset logic
```

```
begin
```

```
if(rst)
```

```
ps<=closed;
```

```
else
```

```
ps<=ns;
```

```
end
```

```
always@(*) //ns & output logic
```

```
begin
```

```
case(ps)
```

```
closed:begin
```

```
ns<=sensor?opening:closed;
```

```
motor_out<=sensor?1:0;
```

```
end
```

```
opening:begin
```

```
ns<=open;
```

```
motor_out<=1'b1;
```

```
end
```

```
open:begin
```

```
ns<=timer?closing:open;
```

```
motor_out<=timer?1:0;
```

```
end
```

```
closing:begin
```

```
ns<=sensor?opening:closed;
```

```
motor_out<=1'b1;
```

```
end
```

```
default:ns<=closed;
```

```
endcase
```

```
end
```

```
endmodule
```

```
module automatic_door_tb();
```

```
reg CLK,RST,Sensor,Timer;
```

```
wire Motor_Out;
```

```
automatic_door dut(CLK,RST,Sensor,Timer,Motor_Out);
```

```
initial
```

```
begin
```

```
CLK=0;
```

```
forever #5 CLK=~CLK;
```

```
end
```

```
initial
```

```
begin
```

```
RST=1'b1; #10;
```

```
RST=1'b0; Sensor=1'b0; Timer=1'b0; #10;
```

```
Sensor=1'b1; #10;
```

```
Sensor=1'b0; #10;
```

```
Timer=1'b1; #10;
```



```
Timer=1'b0; Sensor=1'b1; #10;
```

```
$stop;
```

```
$display("CLK=%0b,RST=%0b,Sensor=%0b,Timer=%0b,Motor_Out=%0b",CLK,RST,Sensor,Timer,Motor_Out);
```

```
end
```

```
endmodule
```

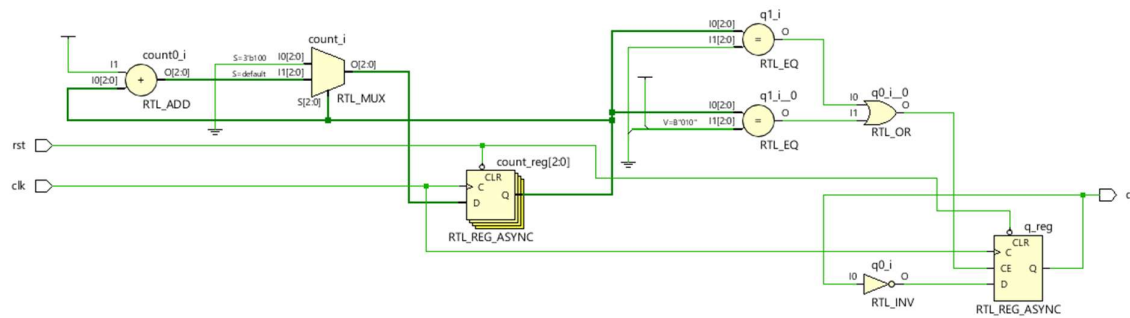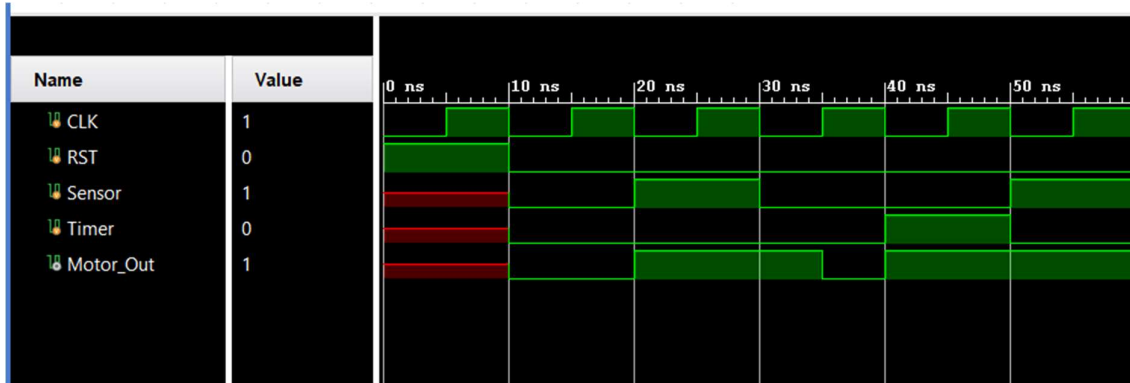

2s COMPLEMENT FSM

```
module complement_2s(
```

```
input clk,
```

```
input rst,
```

```
input in,
```

```
output reg out
```

```
);
```



```
reg [1:0] ps, ns;
```

```
parameter s0 = 2'b00;
```

```
parameter s1 = 2'b01;
parameter s2 = 2'b10;
always@(posedge clk) begin
    if (rst)
        ps<=s0;
    else
        ps<=ns;
    end
    always@(*) begin
        case(ps)
            s0:begin
                ns<=in?s2:s1;
                out<=in?1:0;
            end
            s1:begin
                ns<=in?s2:s1;
                out<=in?1:0;
            end
            s2:begin
                ns<=in?s2:s2;
                out<=in?0:1;
            end
            default:begin
                ns<= ps;
                out<= 0;
            end
        end
    end
end
```

```
endcase  
end  
endmodule
```

```
module complement_2_tb();  
    reg CLK, RST;  
    reg IN;  
    wire OUT;  
    complement_2s dut(.clk(CLK), .rst(RST), .in(IN), .out(OUT));  
    initial begin  
        CLK = 0;  
        forever #5 CLK = ~CLK;  
    end  
    initial begin  
        RST = 1'b1; IN = 1'b0; #10;  
        RST = 1'b0;  
        IN = 1'b0; #20;  
        IN = 1'b1; #20;  
        IN = 1'b0; #20;  
        IN = 1'b1; #20;  
        IN = 1'b0; #20;  
        IN = 1'b1; #20;  
        IN = 1'b0; #20;  
        IN = 1'b1; #100;  
        $stop();  
        $display("time=%0t clk=%b rst=%b in=%b out=%b", $time, CLK, RST, IN, OUT);  
    end  
endmodule
```

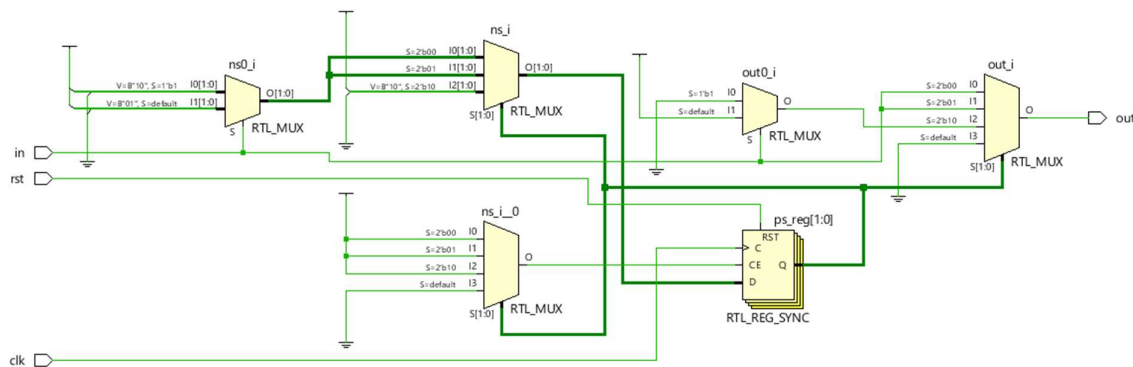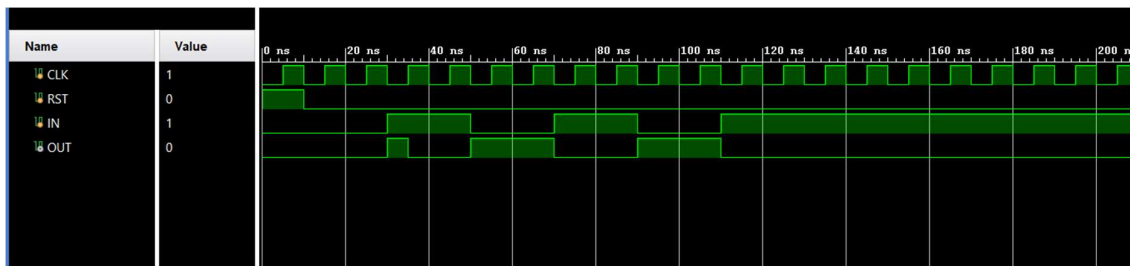

1's COMPLEMENT FSM

```
module complement_1s(clk,rst,in,out);
```

```
input clk,rst,in;
```

```
output reg out;
```

```
reg [1:0]ps,ns;
```

```
parameter s0=2'b00,s1=2'b01;
```

```
always@(posedge clk) //reset logic
```

```
begin
```

```
if(rst)
```

```
ps<=s0;
```

```
else
```

```
ps<=ns;
```



```

end
always@(*)
begin
case(ps)
s0:begin
ns<=in?s0:s1;
out<=in?0:1;
end
s1:begin
ns<=in?s0:s1;
out<=in?0:1;
end
endcase
end
endmodule

```

```

module complement_1s_tb();
reg CLK,RST,IN;
wire OUT;
complement_1s dut(CLK,RST,IN,OUT);
initial
begin
CLK=0;
forever #5 CLK=~CLK;
end
initial

```

```

begin

RST=1'b1; #10; RST=1'b1;

IN=1'b0; #10; IN=1'b0; #10;

IN=1'b1; #10; IN=1'b0; #10;

IN=1'b1; #10; IN=1'b1; #10;

IN=1'b0; #10;

$stop;

$display("CLK=%0b,RST=%0b,IN=%0b,OUT=%0b",CLK,RST,IN,OUT);

end

endmodule

```

